



**UNIVERSITY OF TEHRAN**  
**Electrical and Computer Engineering Department**  
**ECE 367, Digital Logic Circuits – Fall 1397**  
**Computer Assignment 6**  
**RTL Processing Element Design and Implementation**  
**Due week 15 of the semester**

---

Taylor series is one of well-known methods to compute mathematical functions such as  $\sin(x)$ ,  $\cos(x)$ ,  $\exp$ , etc. In this problem you are to design a sequential circuit that computes an approximation of  $\tan x$  using the first 8 terms of its Taylor expansion. The numbers  $B_{2n}$  are Bernoulli numbers.

$$\tan x = \sum_{n=1}^{\infty} \frac{B_{2n}(-4)^n (1-4^n)}{(2n)!} x^{2n-1} = x + \frac{x^3}{3} + \frac{2x^5}{15} + \dots \quad \text{for } |x| < \frac{\pi}{2}$$

$$\tan x = x + \frac{1}{3}x^3 + \frac{2}{15}x^5 + \frac{17}{315}x^7 + \frac{62}{2835}x^9 + \dots$$

The algorithm you chose to implement should use an array multiplier and a ROM for series coefficients.

Shown below is the block diagram of the module approximating  $\tan()$ . The module accepts a 16-bit fixed point value on  $x$  between 0 and  $\pi/2$  after  $start$  is asserted. After that, computation is started. During the computation, the  $busy$  signal is asserted. After the completion of the computation, the result becomes available on output  $y$ ,  $busy$  is deactivated, and  $ready$  is issued.

As mentioned,  $x$  is between 0 and  $\pi/2$ , and all numbers are represented in 16-bit fixed point format. In addition, a 16-bit fixed point adder and a 16-bit fixed point array multiplier are available as datapath components. The series coefficients must be pre-calculated and stored in a combinational lookup table. The table has four address lines and a 16-bit data output.

- A) Generate a ROM in Quartus II for the required memory of factorial calculations.
- B) Design the datapath of module  $\tan(x)$ , and implement it in Quartus II.
- C) Write a Verilog description for the controller of module  $\tan(x)$ .
- D) Complete the datapath and controller of your circuit and develop a testbench for it.

